

2ND SEMESTER EXAMINATION, APRIL - 2005

BASIC ELECTRONICS

Full Marks - 70

Time : 3 Hours

The figures in the right hand margin indicate full marks for the questions.

Question No. 1 is compulsory and answer any five from the rest.

Assume suitable data if not mentioned. Symbols carry their usual meaning.

1. Answer the following briefly : 2×10


(a) Do the following number conversions :

(i) $A3E89_{16}$ to octal


(ii) $82B_8$ to hexadecimal.

P.T.O.

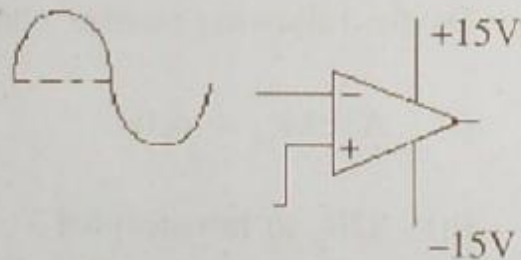- (b) Subtract the following binary numbers :
- (i) $1100 - 1001$
- (ii) $11010 - 10111$.
- (c) Express -85 in 8-bit sign-magnitude 1's and 2's complement form.
- (d) Add 56 and -27 using 2's complement.
- (e) The resistance of a semiconductor material decreases with an increase in temperature - Justify this statement.
- (f) Distinguish between Zener breakdown and Avalanche breakdown. Which of these can be used in high voltage applications ?
- (g) Draw the output waveform for the following circuit :



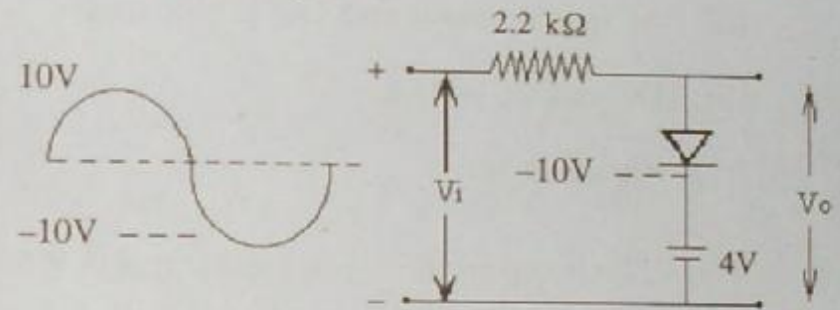- (h) Bring out the differences between BJT & FET ?
- (i) Draw and scale the output waveform for the following circuit :



- (j) If $\sqrt{41}I_b = 5I_b$, find the value of b .

2. Radiation falls on a semiconductor specimen that is uniformly illuminated, and a steady state is reached. At $t = 0$, the light source is switched off. Sketch the minority carrier concentration as a function of time for $t \geq 0$. Define all the symbols in your equation describing the sketch. 10
3. A crystal diode having an internal resistance $r_f = 20\Omega$ is used for half-wave rectification. If the applied voltage is $v = 50 \sin\omega t$ and the load

resistance is $R_L = 800\Omega$, determine the following :

10


(i) I_m , I_{dc} and I_{rms} .

(ii) AC power input and DC power output.


(iii) DC output voltage.

(iv) Ripple factor.

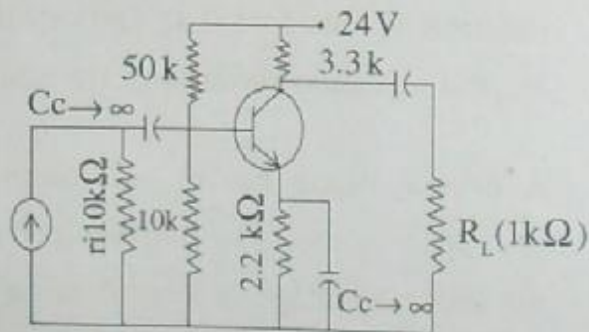4. The BJT shown in the figure below has $\beta = 50$. All bypass and coupling capacitors are assumed to have zero reactance at the signal frequency. Find the quiescent conditions (V_{CEQ} , I_{CQ}), the small signal equivalent circuit the current, gain and input impedance seen by the current source i_c . 10




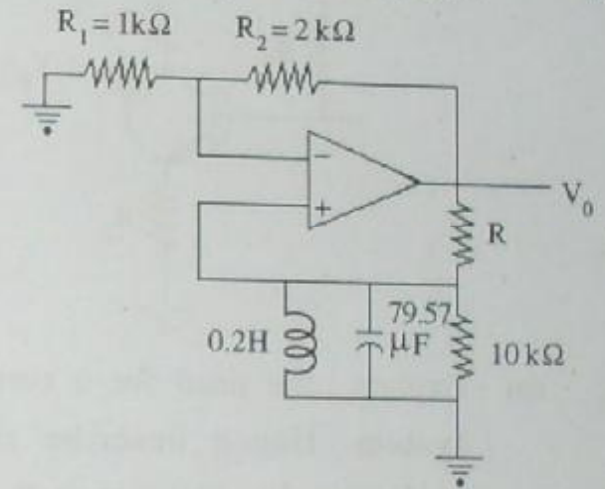5. Consider the op-amp to be ideal. What is the value of R for which oscillations will be sustained? What is the frequency of oscillation? 10



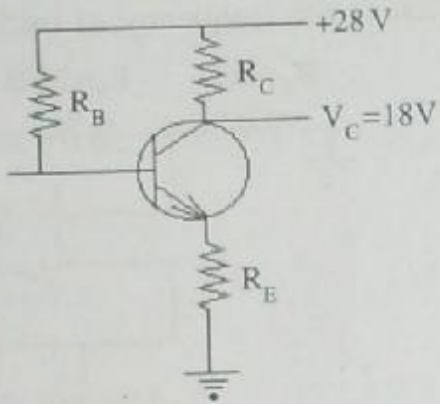6. (i) Convert the following expression to canonical SOP form : 5
 $(\bar{A} + C).(A.B + A.B + A.C)$
- (ii) Convert the following expression to canonical POS form : 5
 $A + A.B + \bar{A}.C$
7. For the emitter bias configuration of Figure below with the specifications : $I_{CQ} = (1/2) I_{Csat}$, $I_{Csat} = 8\text{ mA}$,

$V_C = 18V$ and $\beta = 110$, determine the value of R_C , R_E and R_B . 10



8. (a) Explain the need for a communication system. Hence describe the role of modulation demodulation in it. 5

(b) What is the input impedance of an ideal voltmeter? Why? Explain the CRO as a voltmeter? 5