

Fourth Semester Examination, April - 2005

BASIC ELECTRONICS

Full Marks : 70

Time : 3 Hours

Answer Question No. 1 which is compulsory and any five questions from the rest.

The figures in the right-hand margin indicate marks for the questions.

1. Answer the following : 2×10

- (a) If the depletion width of a p-n junction with doping levels of  $N_A = 10^{16}/\text{cm}^3$  and  $N_D = 10^{18}/\text{cm}^3$  is  $x_d$ , what distance does the depletion region penetrate into the n-side of the junction ?

0.5 8d

P.T.O.

- (b) What is the value of the current  $I$  in the following circuit (Fig. 1) assuming  $V_Z = 5.6V$  and  $V_D = 0.7V$ .

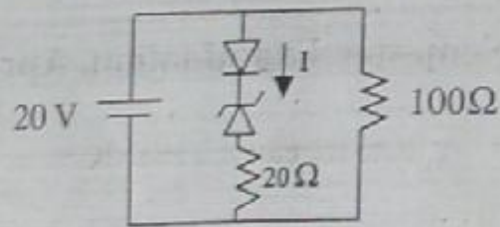


Figure 1

- (c) If  $292_{10} = 1204_b$ , determine the value of  $b$ .  $6$
- (d) Convert the decimal number 359 to its octal equivalent.  $547$
- (e) Find the node voltage  $V_2$  and  $I_C$  for the following circuit (Fig. 2). Take  $\beta$  to be very high.

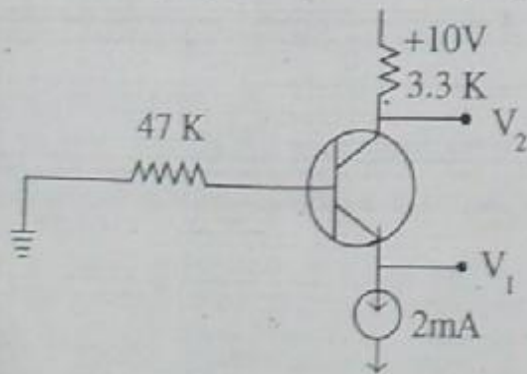


Figure 2

- (f) An enhancement type NMOS transistor with  $V_T = 2V$  has its source terminal grounded and its gate is given 3V. In what region of operation the device operate for  $V_D = 0.5V$  and  $V_D = 1V$ ?
- (g) Draw and scale the output waveform of the following circuit (Fig. 3) if a sinewave of 10V p-p is applied to the following circuit.

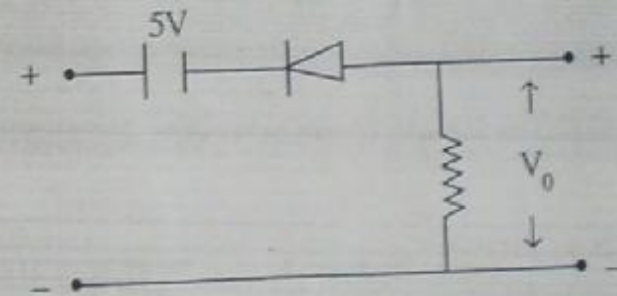


Figure 3

- (h) A 10V forward voltage is applied to a silicon diode in series with a load of  $10K\Omega$ . Draw the dc load line and find its slope.
- (i) If each inverter in the following figure (Fig. 4) has a propagation delay of 10ns, determine the waveshape of the output waveform  $V_O$ . What is its frequency?

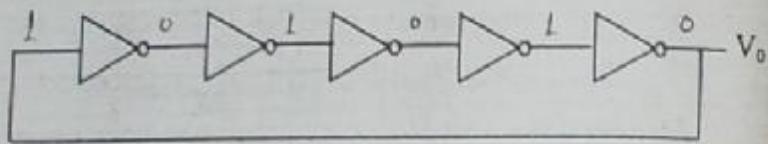


Figure 4

(j) Apply DeMorgan's law to the following expression :

$$\overline{AB(C+\bar{D})}$$

2. A germanium diode displays a forward voltage of 0.25V at 10mA current at room temperature(300°K). Estimate the reverse saturation current( $I_s$ ) assuming unity ideality factor. Calculate the bias voltage needed for diode currents of 1mA and 100mA. Also estimate the values of  $I_s$  and diode forward current at 0.25V at 30°C above room temperature. 10
3. A bridge rectifier uses a diode with forward resistance of 5Ω each. Transformer secondary resistance is 5Ω and the secondary voltage is 30V(rms). Determine the dc output voltage for  $I_{dc} = 200\text{mA}$  and the rms value of the output ripple voltage. 10

4. For both the circuits shown below (Fig. 5a, 5b), calculate  $I_B, I_C$  and  $V_{CE}$ . Take  $V_{cc} = 12\text{V}$ ,  $V_{BE} = 5\text{V}$ ,  $R_B = 86\text{K}$ ,  $R_C = 1\text{K}$ ,  $R_E = 1\text{K}$ ,  $R_F = 80\text{K}$ ,  $V_{BE} = 0.7\text{V}$  and  $\beta = 120$ .

(a)

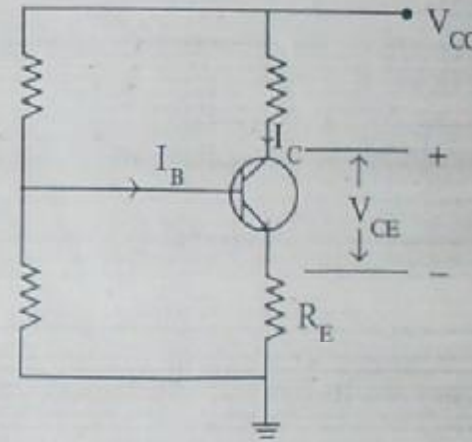


Figure 5a

(b)

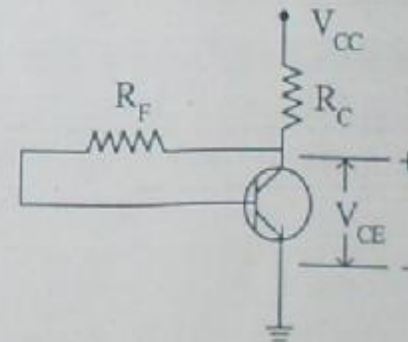


Figure 5b

0-0562

6. Derive the transfer characteristics in terms of  $R$ ,  $I_s$  ( $I_s$  being the reverse saturation current of the transistor) and  $V_T$ . Assume  $n = 1$ . (For the circuit shown in Fig. 6). 10

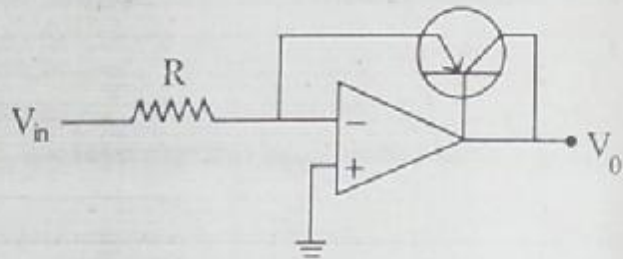


Figure 6

7. (a) Bring out the essential differences between an analog communication system and a digital communication system. 5
- (b) What type of time base is used in a CRO? Explain with a neat sketch. 5