

Total number of printed pages – 8

B. Tech

BENG 1105

First Semester Examination – 2007

**BASIC ELECTRONICS**

Full Marks – 70

Time : 3 Hours

*Answer Question No. 1 which is compulsory  
and any five from the rest.*

*The figures in the right-hand margin  
indicate marks.*

1. Answer the following questions : 2 × 10
- (a) Distinguish metals from semiconductors with reference to position of Fermi level.
- (b) What is Zener Breakdown ? Give two reasons.

P.T.O.

(c) Derive the expression of  $I_C$  versus  $I_B$  for a CE transistor configuration.

(d) Convert  $(0.275)_{10}$  into binary equivalent and  $(100101)_2$  into decimal equivalent.

(e) Derive the expression for amplification factor  $\mu$  of FET.

(f) Draw the circuit of an OPAMP integrator.

(g) Write two disadvantages of positive feedback.

(h) Give two reasons of using modulation.

(i) Draw frequency response of a practical operational amplifier.

(j) Define modulus of an n-bit counter. What is the modulus of a decade counter ?

2. (a) Name a p-n diode that is used in tuned circuits. Explain its operation. 2

(b) Draw the circuit of a double ended clipper using ideal p-n diodes which limits the outputs from +3 Volt to -3 Volt for sinusoidal input of amplitude 5 Volt. 3

(c) Draw output waveform  $V_o$  for the biased clamping circuit shown in Fig. 1. Assume  $V_i = 5V$  square wave. What happens to the output waveform when the diode is reversed ? 5

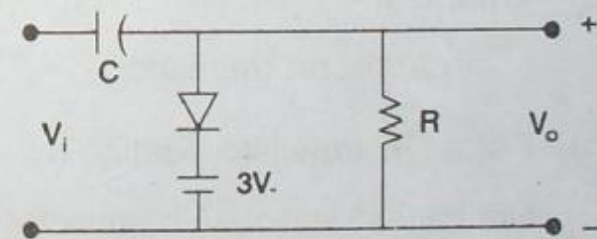


Fig. 1

3. (a) In the circuit shown in Fig. 2, find the minimum value of  $R_x$  for which the transistor remains in saturation. Assume that a silicon transistor with  $V_{BE, sat} = 0.8$  volt,  $\beta = h_{FE} = 100$  and  $V_{CE, sat} = 0.2$  V is used in the circuit. 5

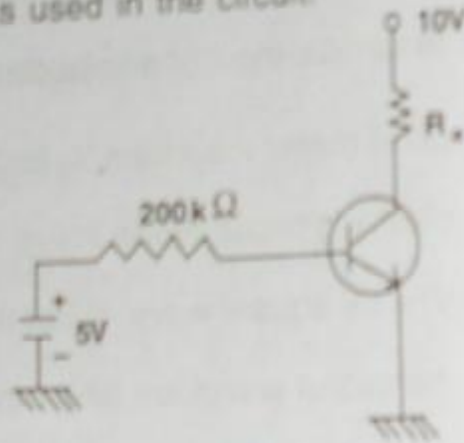


Fig. 2

- (b) What is the collector current relative to  $I_{CO}$  in a silicon transistor? 2
- (c) For a CE transistor, define  $h_{FE}$  and  $h_{FE}$ . Derive the relationship between  $h_{FE}$  and  $h_{FE}$ . 3

4. (a) For the circuit shown in Fig. 3, find the collector current  $I_C$ . Assume that a silicon transistor with  $h_{FE} = 98$  is used. 5

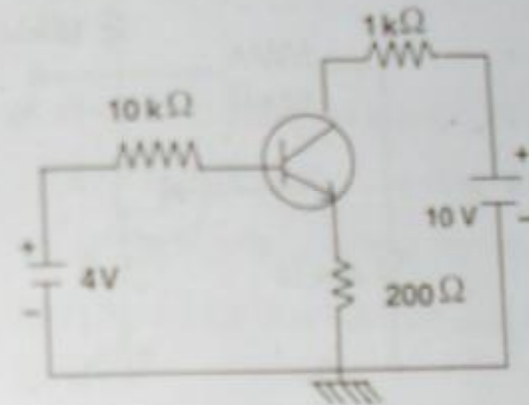


Fig. 3

- (b) Describe the principle of operation of enhancement type MOSFET with suitable diagrams. Sketch its transfer characteristics. 5
5. (a) Calculate the voltage gain of the circuit shown in Fig. 4, if the input is given

between gate and ground. The FET parameters are  $\mu = 30$  and  $r_d = 5 \text{ K ohms}$ .

5

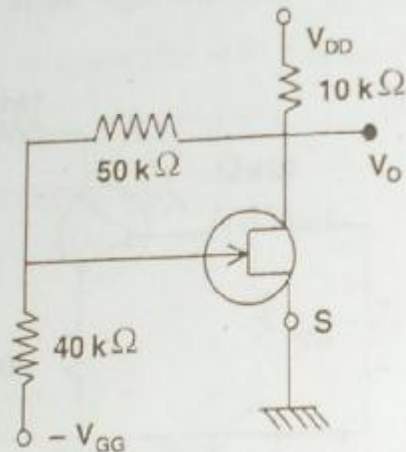


Fig. 4

(b) The gain of an amplifier changes from a value of  $-800$  by  $10\%$ . Calculate the gain change of the amplifier used in a feedback circuit with  $\beta = -\frac{1}{20}$ .

5

6. (a) Sketch the circuit diagram of a modulo 10 counter. Explain the operation.

5

(b) Using Boolean algebra, verify

$$\overline{AB + BC + CA} = \overline{A} \overline{B} + \overline{B} \overline{C} + \overline{C} \overline{A} \quad 2$$

(c) Implement EXOR logic using NOR gates only.

3

7. (a) Draw the schematic block diagram of the basic OPAMP with inverting and non inverting inputs. Indicate its equivalent circuit. List six characteristics of an ideal OPAMP.

5

(b) Sketch the output of a differentiator circuit using an OPAMP, if the input is a square wave of  $10 \text{ MHz}$ . Assume the time constant of the circuit to be  $1 \text{ milli seconds}$ .

5

8. (a) Derive the relationship between the output power of an AM transmitter and the depth of modulation, and plot this as

a graph for values of the modulation index from zero to maximum. A suppressed zero graph is misleading in this instance, and must not be used. 5

- (b) A certain transmitter radiates 9 kW with the carrier unmodulated, and 10.125 kW when the carrier is sinusoidally modulated. Calculate the modulation index. If another sine wave, corresponding to 40% modulation is transmitted simultaneously, determine the total radiated power. 5