

**Total number of printed pages – 7**      **B. Tech**  
**CPES 5201**

**Fourth Semester Examination – 2008**

**NETWORK THEORY**

**Full Marks – 70**

**Time : 3 Hours**

*Answer Question No. 1 which is compulsory  
and any **five** from the rest.*

*The figures in the right-hand margin  
indicate marks.*

1. Answer the following questions :      2×10
- (i) Give at least three properties of parallel resonance circuit.
  - (ii) What are half power frequency points ? Explain.



- (iii) What is the difference between an ideal filter and a practical filter ?
- (iv) Give the properties of a filter.
- (v) What are even and odd functions ? Give examples.
- (vi) What is the nature of the impulse response of an RL circuit ?
- (vii) For the band pass filter what is the normal characteristic impedance ?
- (viii) What is the value of ramp function at  $t=0$  ?
- (ix) What is the reciprocal of a driving point function ?
- (x) State final value theorem.

**P.T.O.**

**CPES 5201**

**2**


**Contd.**

2. (a) Define the following network functions with reference to a 2-port network : 4

(i) driving point impedance

(ii) transfer impedance.

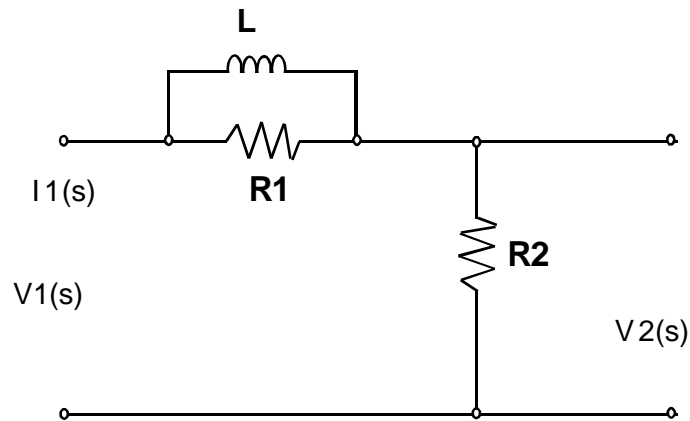(b) For the given network, find the transfer functions  $G_{21}(s)$ ,  $Z_{21}(s)$  and driving point impedance  $Z_{11}(s)$ . 6



3. (a) What do you understand by : 4

(i) zeros of a function, and

(ii) zeros of transmission.

(b) What information do poles and zeros provide in respect of a network to which they relate ? Draw pole and zeros for : 6

$$\frac{s^2 + 3s + 2}{s^2 + 7s + 12}$$

And evaluate  $v(t)$  either analytically or by making use of pole-zero diagram.

4. (a) Derive the expression of Z-parameters in terms of other parameters. 5

(b) Calculate the Z-parameters, if the values of other parameters are given below : 5

(i)  $A = 2$ ,  $B = -1$ ,  $C = 3$  and  $D = -2$

(ii)  $h_{11} = 1$ ,  $h_{12} = -2$ ,  $h_{21} = -3$ ,  $h_{22} = 2$

(iii)  $Y_{11} = 1/3$ ,  $Y_{12} = 2/3$ ,  $Y_{21} = -1/3$ ,  $Y_{22} = 1/6$

5. (a) Draw and discuss the profile of circuit parameters with frequency in a parallel resonant circuit. 3
- (b) Derive the relationship between Bandwidth, Detuning Factor, Quality factor, Impedance and selectivity of a parallel resonant circuit. 3
- (c) A current source, having an internal resistance of  $10\text{ K}\Omega$  feeds a tank circuit containing a coil (having  $L_C = 200\text{ mH}$ ,  $R_C = 10\ \Omega$ ) in parallel to a capacitor of  $100\ \mu\text{F}$ . Find the frequency of resonance and Q factor. 4
6. (a) Discuss the basic concept of working of low pass and high pass filters using reactive elements. 3


- (b) Analyze a prototype High Pass Filter. 3
- (c) Design the T and  $\pi$  section of a prototype High Pass Filter having cut-off frequency of  $20\text{ kHz}$  and design impedance of  $450\ \Omega$ . Also find its characteristic impedance and phase constant at  $25\text{ kHz}$  as well as determine the attenuation at  $4\text{ kHz}$ . 4
7. (a) Represents the given impedance function using Cauer-I form. 5

$$Z(s) = \frac{s^2 + 1}{s^2 + 2}$$

- (b) Synthesize the Foster-II form of given admittance function 5

$$Y(s) = \frac{s^2 + 5}{s^2 + 3}$$

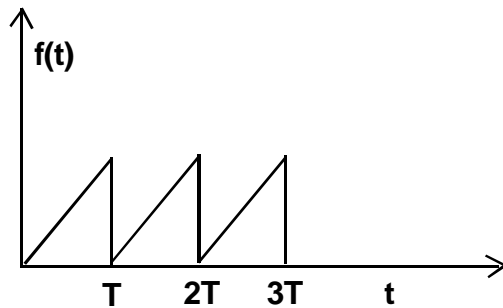8. (a) Determine the effective value of  $f(t)$  of the waveform shown in the figure below. 5



- (b) Obtain the Fourier coefficients for the function given by 5  
 $f(t) = (t + \pi)$  when  $-\pi < t < \pi$ ;  $f(x+2\pi) = f(x)$

---